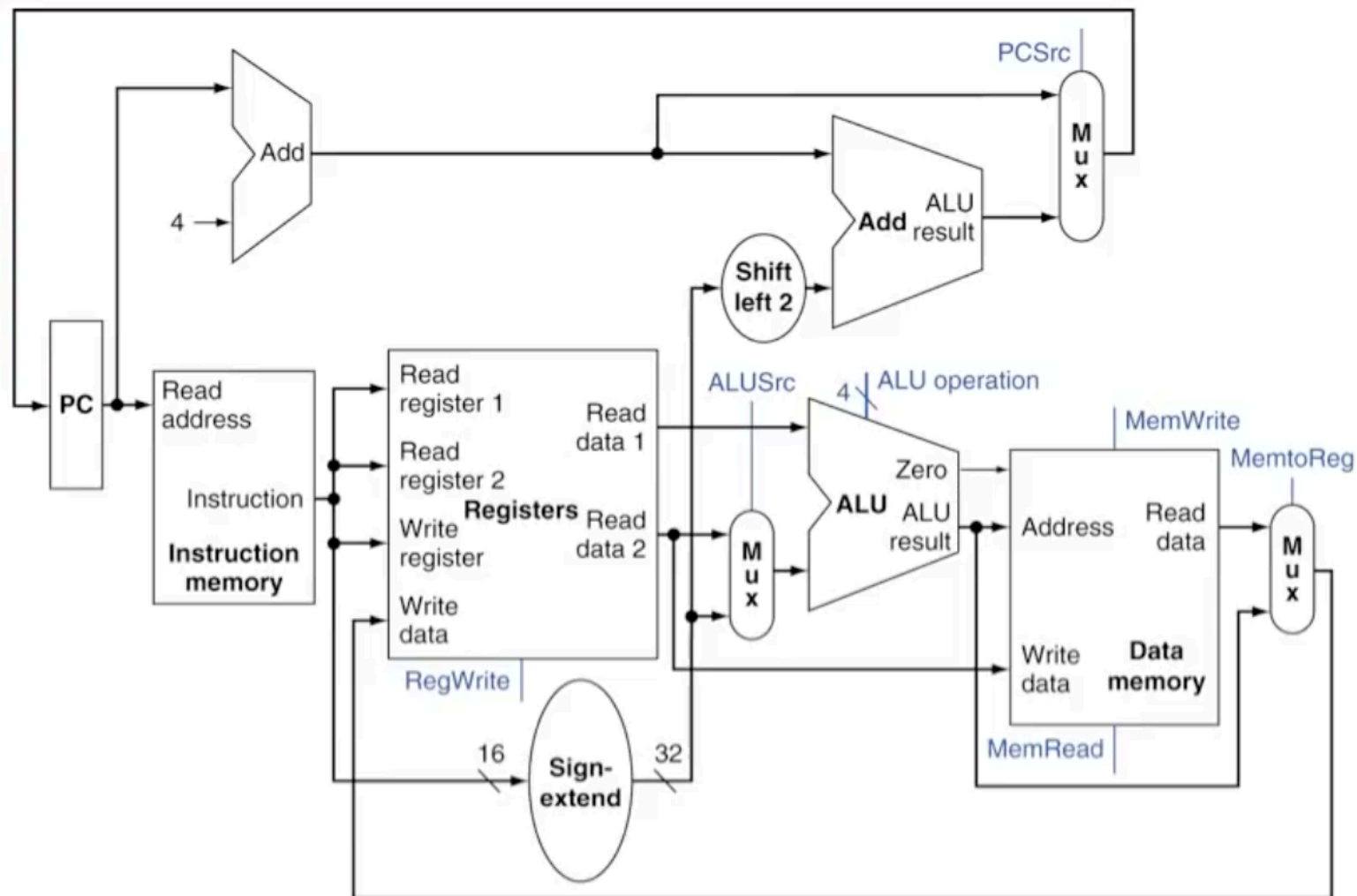



Computer Architecture

Processor Pipelining

Single-cycle datapath



Single-cycle datapath

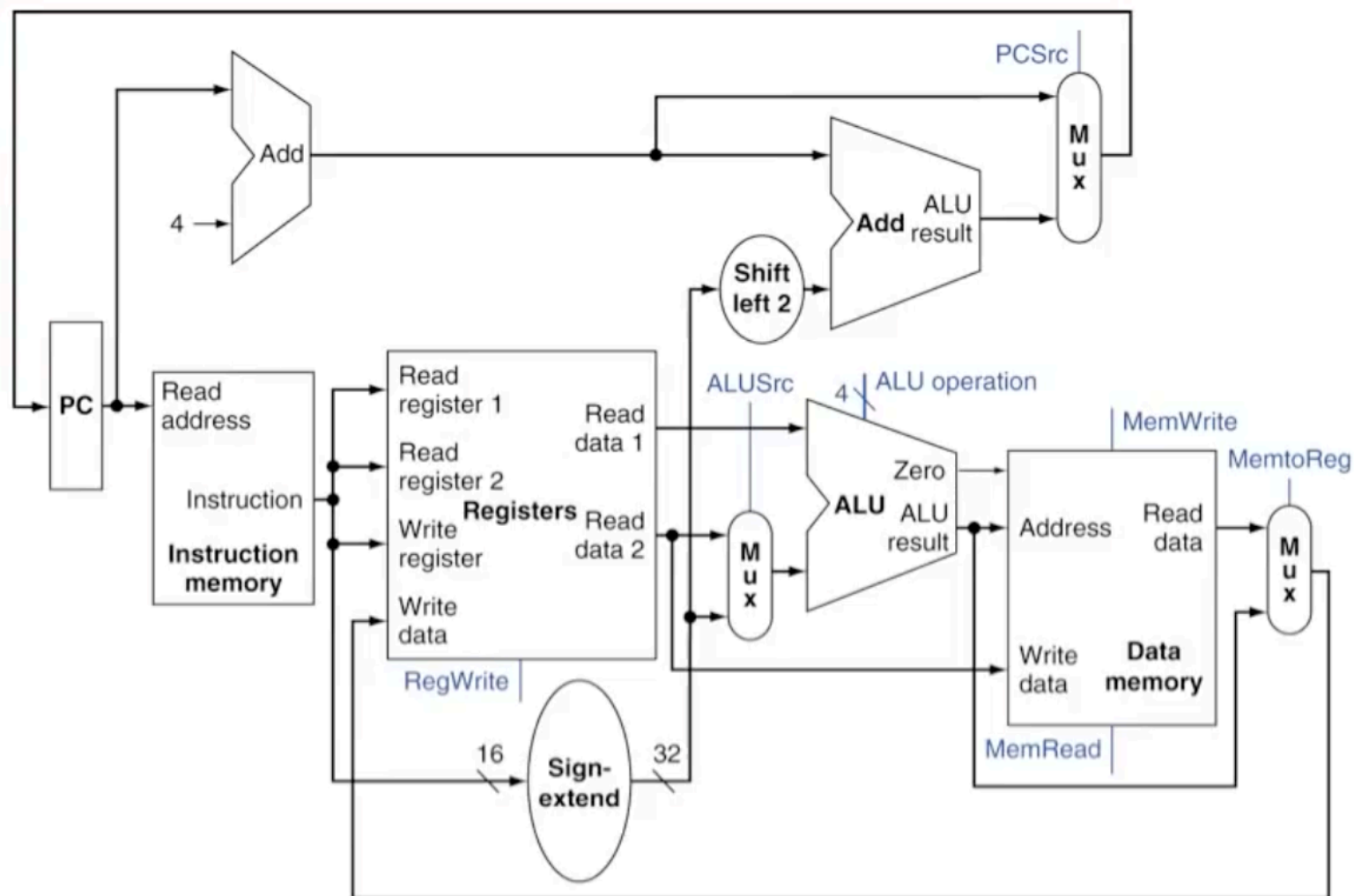


The speed of a processor is determined by what?

A. slower instruction


B. faster instruction

Single-cycle datapath


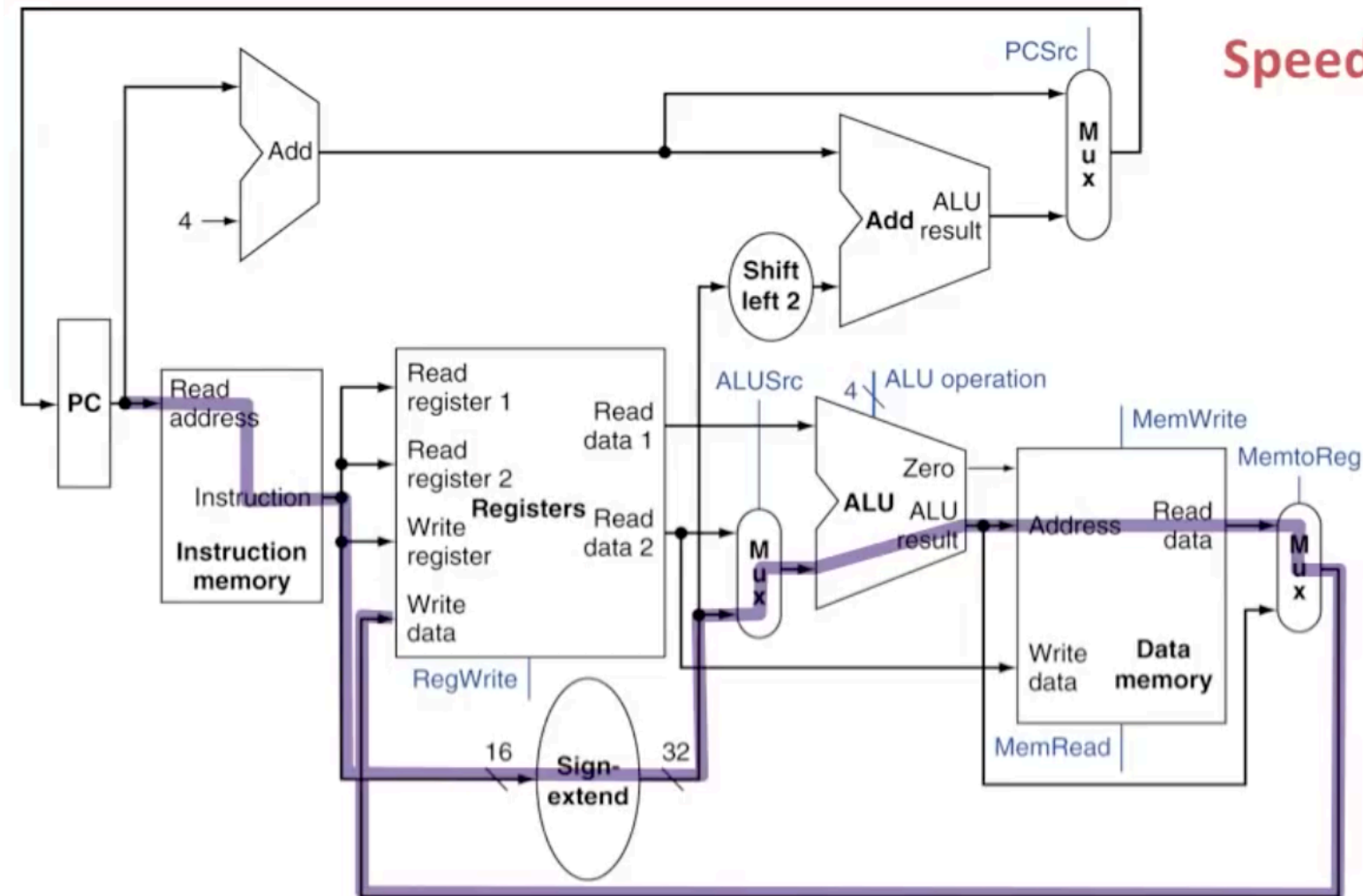


Speed limited by the slowest path

Single-cycle execution times

 



Single-cycle execution times

  

Wasted time.
The instruction doesn't
need this time

YouTube

Single-cycle execution times

 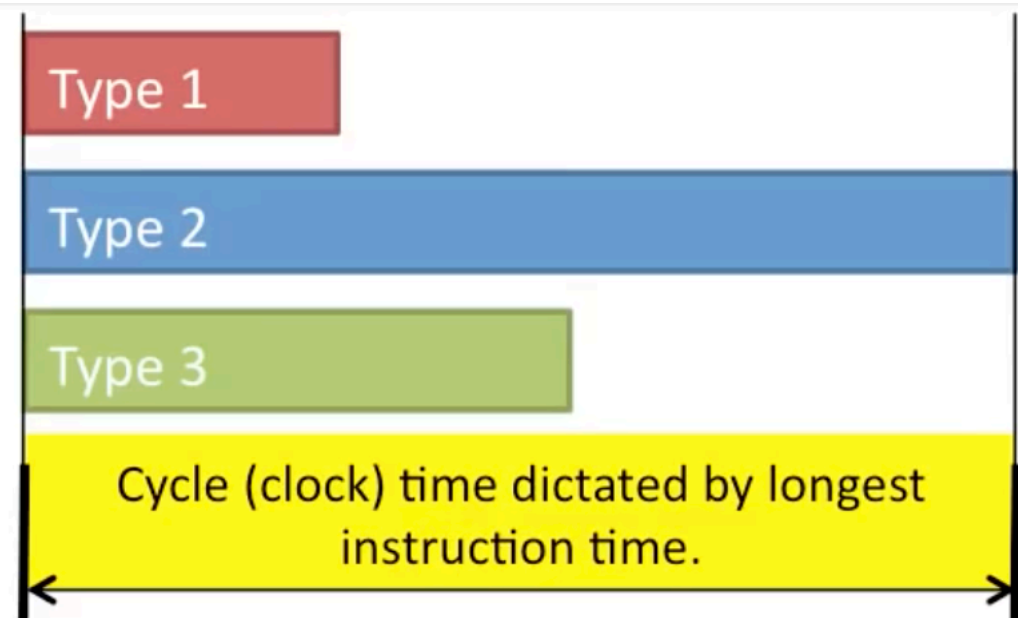

- Slowest instruction determines cycle time
- Much of the time is wasted

Wasted time.
The instruction doesn't
need this time


The Solution??? Multi-cycle processor

The Solution??? Multi-cycle processor

- Let the **fastest instruction determine the clock cycle**
- And have slower instructions take multiple cycles


The Solution??? Multi-cycle processor

 - Let the **fastest instruction determine the clock cycle**
- And have slower instructions take multiple cycles




The Solution??? Multi-cycle processor

 - Let the **fastest instruction determine the clock cycle**
- And have slower instructions take multiple cycles



The Solution??? Multi-cycle processor

 - Let the **fastest instruction determine the clock cycle**
- And have slower instructions take multiple cycles



But very complicated to keep track of how long each instruction runs.

Much less wasted time



Which of the following statement is NOT necessarily TRUE?

- A. In a single-cycle processor, the longest instruction determines the speed of the processor.
- B. In a multi-cycle processor, the clock cycle is determined by the fastest instruction.
- C. In a pipelined processor, the slowest instruction determines the speed of the processor.
- D. None of the above

Which of the following statement is NOT necessarily TRUE?


A. In a single-cycle processor, the longest instruction determines the speed of the processor.

B. In a multi-cycle processor, the clock cycle is determined by the fastest instruction.


C. In a pipelined processor, the slowest instruction determines the speed of the processor.

D. None of the above


MIPS 5 stage pipeline

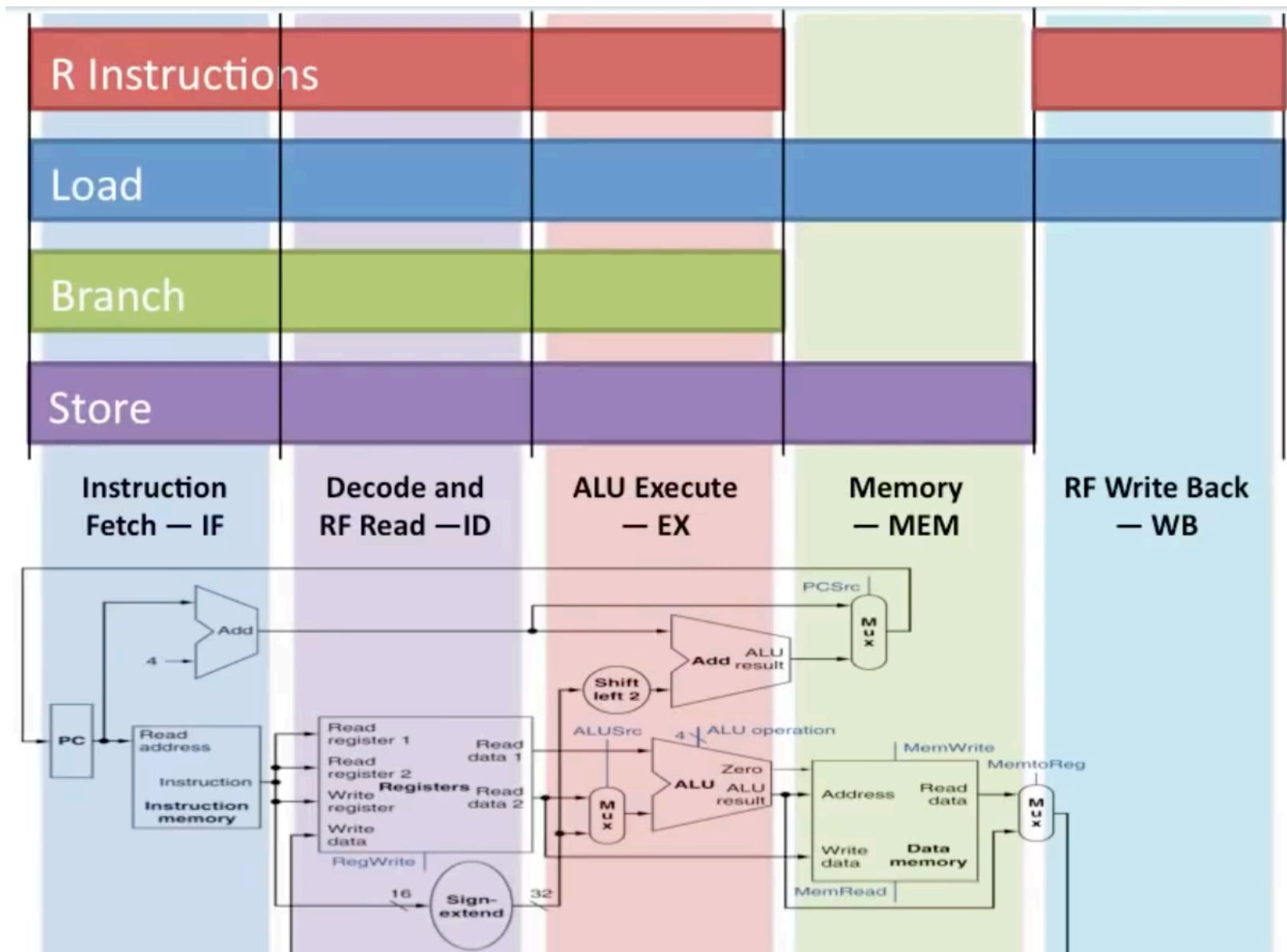

MIPS 5 stage pipeline

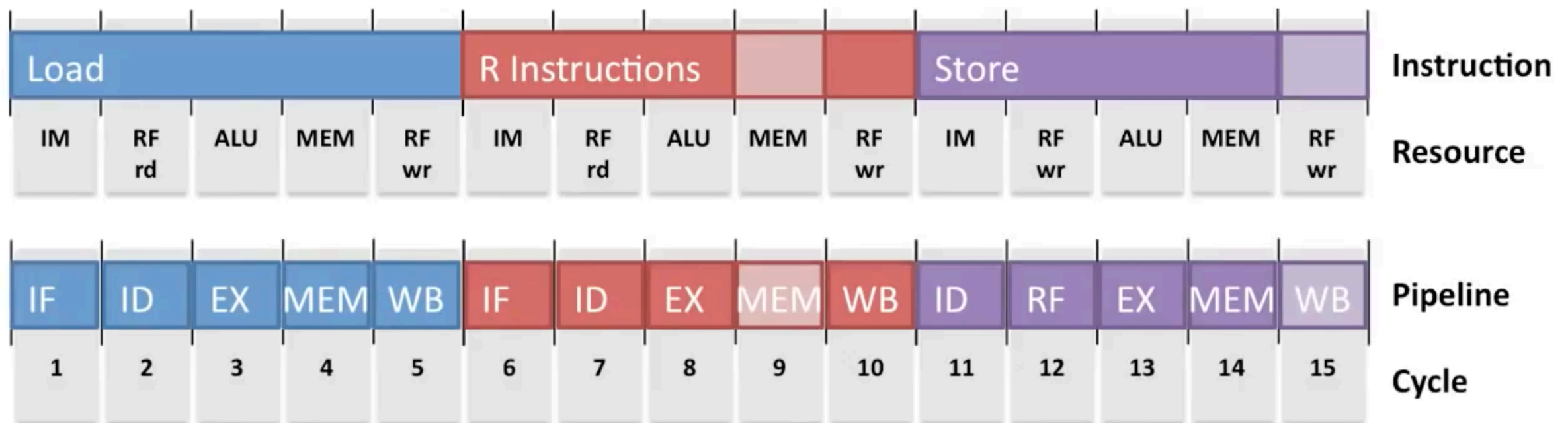


MIPS 5 stage pipeline

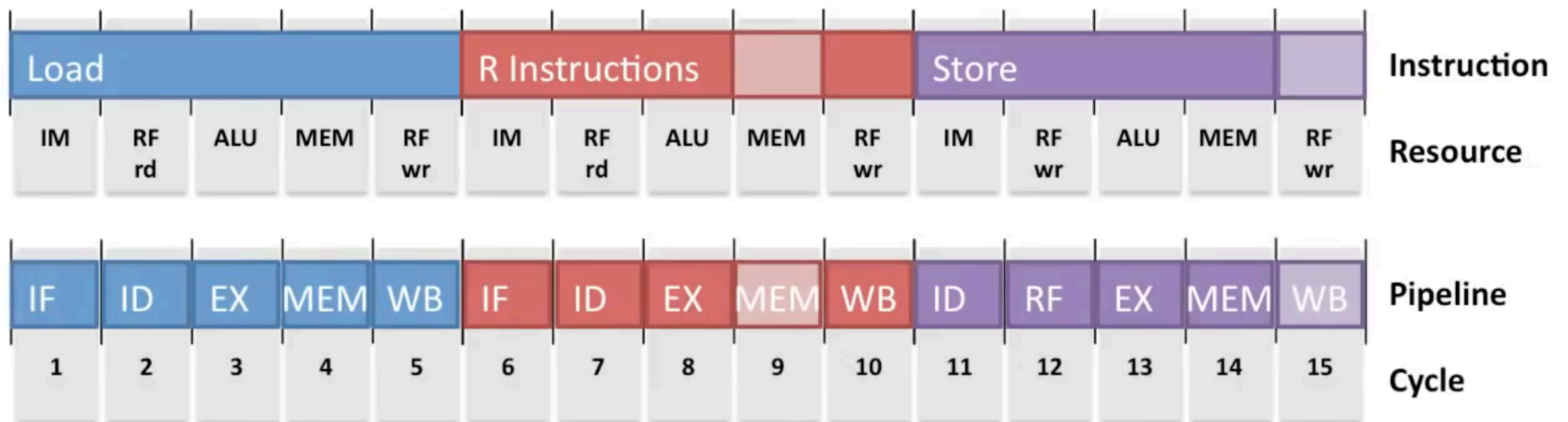

What is the ALU doing in cycle 7?

Pipelining to do work in parallel...

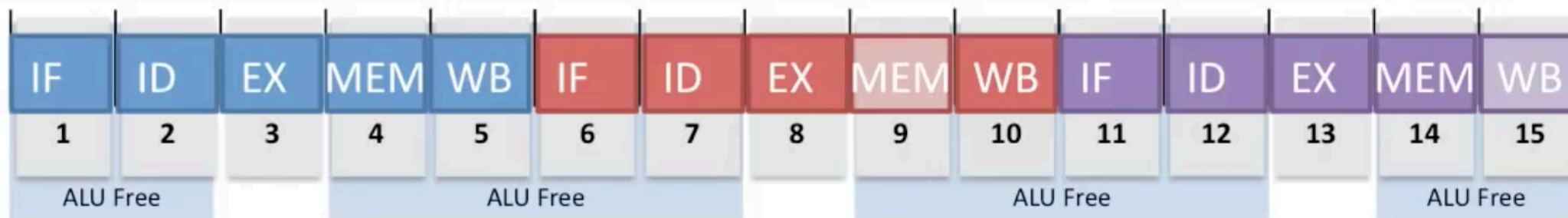


This is what we want from pipelining:

Use all parts of the processor for different instructions at the same time.

(This is why dividing up instructions into 5 phases was helpful.)

Differentiate throughput and latency.

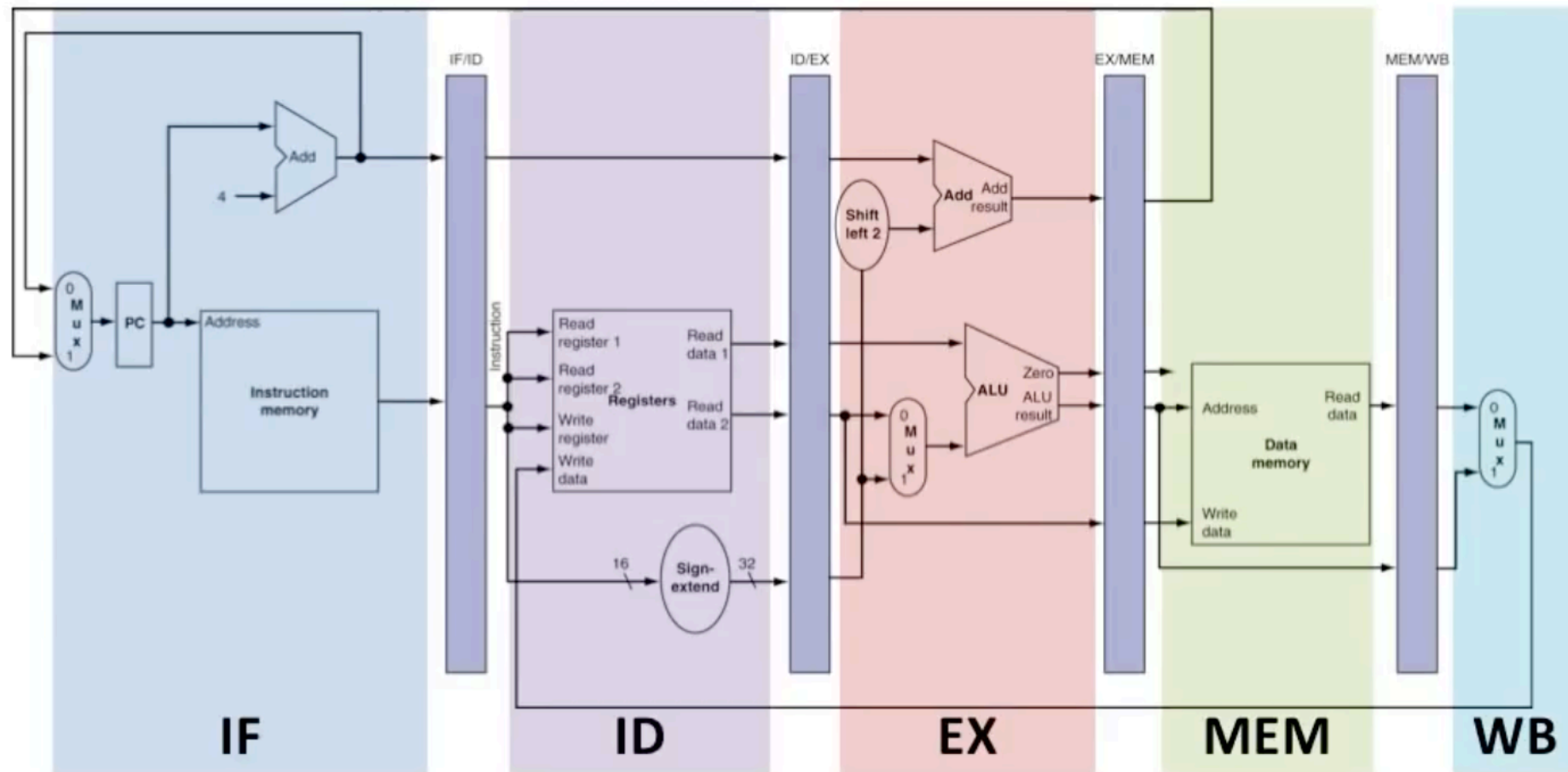Why is there a need to put pipeline registers?



- What are the control signals for add, load, and bne?
- What do they do?
- Fill in the table below specifying the value and meaning. (For ALUOp you can write the name of the op such as “Add”.)

| | | EX | | | MEM | | | WB | |
|------|------------|---------|---------|--------|--------|-----------|----------|-----------|----------|
| | Inst. Type | ALU Src | Reg Dst | ALU Op | Branch | Mem Write | Mem Read | Mem toReg | RegWrite |
| add | | | | | | | | | |
| load | | | | | | | | | |
| bne | | | | | | | | | |

